

Switch level programming in Verilog

The switch primitives (transistor models) are: `nmos`, `pmos`, `cmos` (for the transmission gate)

Usage:

```
nmos (drain, source, gate);
```

```
pmos (drain, source, gate);
```

Transmission gate:

```
cmos (w, datain, ncontrol, pcontrol);
```

is equivalent to:


```
nmos (w, datain, ncontrol);
```

```
pmos (w, datain, pcontrol);
```

Verilog signal strength levels:

Strength Level	Specification Keyword
7 Supply Drive	<code>supply0</code> <code>supply1</code>
6 Strong Pull	<code>strong0</code> <code>strong1</code>
5 Pull Drive	<code>pull0</code> <code>pull1</code>
4 Large Capacitance	<code>large</code>
3 Weak Drive	<code>weak0</code> <code>weak1</code>
2 Medium Capacitance	<code>medium</code>
1 Small Capacitance	<code>small</code>
0 Hi Impedance	<code>highz0</code> <code>highz1</code>

Examples:

 


Two buffers that have output

A : `pull1`

B : `supply0`

 Since `supply0` is stronger than `pull1`,
Output C takes value of B.



Two buffers that has output

A : `supply1`

B : `large1`

Since `supply1` is stronger than `large1`,
Output C takes the value of A

CMOS not gate:

```
module not_switch (out, in);  
    output out;  
    input in;  
  
    supply1 power;  
    supply0 ground;  
  
    pmos (out, power, in);  
    nmos (out, ground, in);  
  
endmodule
```

CMOS nand gate:

```
module nand_switch(out, a, b);  
    input a, b;  
    output out;  
  
    supply0 vss;  
    supply1 vdd;  
    wire net1;  
  
    pmos p1 (out, vdd, a);  
    pmos p2 (out, vdd, b);  
    nmos n1 (net1, vss, a);  
    nmos n2 (out, net1, b);  
  
endmodule
```