The goal of this assignment is to get your software tools ready and write some "helloworlds".


Task 1

Download Logisim from http://www.cburch.com/logisim/ If the *.exe file does not open, try *.jar


Start Logisim. Go to Help/Tutorial. Read throug the Beginner's tutorial.

Build a circuit that computes a Boolean function $y=\bar{a}\,\bar{b}\,\bar{c}+a\,\bar{b}\,\bar{c}+a\,\bar{b}\,c$ by completing the following steps.


Go to Project -> Analyze circuit

 


Add the input variables

 


Add the output variable

 


Insert the equation

 

 
Now you can also look at the truth table:



 Press "Build circuit" and choose "Use Two-Input Gates Only"



This is what you should get:

 

Now you can change inputs and observe the output.

Install Icarus Verilog from http://iverilog.icarus.com/

Icarus Verilog for Windows: http://bleyer.org/icarus/

Go to the iverilog directory


```
06:48
                <DIR>
                <DIR>
                <DIR>
                <DIR>
                                 gtkwave
                                 carus Verilog.url
                <DIR>
                                 include
                <DIR>
                                 install
                <DIR>
                <DIR>
                <DIR>
06:48
06:47
```

There's a subdirectory "samples" that contains a few sample files and a quick start guide.

cd samples

Open and read the file hello.vl

 The Notepad++ editor provides a proper syntax highlighting for Verilog files



Compile the file:

iverilog -o hello hello.vl

The program will create the output file "hello". Run this program:

vvp hello

```
Write a Verilog code that computes a Boolean function y = \bar{a}\bar{b}\bar{c} + a\bar{b}\bar{c} + a\bar{b}\bar{c}
`timescale 1ns/1ns
module sillyfunction (input a, b, c,
                            output y);
      assign y = ~a & ~b & ~c |
                    a & ~b & ~c |
                    a & ~b & c;
endmodule
Save it in a file silly.v
Then write a testbench (in the same file) to test the sillyfunction module
module sillyfunction_tb ();
      reg a, b, c;
      wire y;
      // instantiate device under test
      sillyfunction dut (a, b, c, y);
      initial begin
            $dumpfile("silly.vcd");
            $dumpvars(0, dut);
      end
      // apply inputs one at a time
      initial begin
            a = 0; b = 0; c = 0; #10;
            c = 1;
                                      #10;
```

b = 1; c = 0;

c = 1;

#10;

#10;

end

endmodule

Compile the source file:

iverilog -o silly silly.v

This should create the output file "silly". Run this program:

vvp silly

The program will create a dumpfile silly.vcd which you can analyse in gtkwave:

gtkwave silly.vcd

You should get the following waveform

